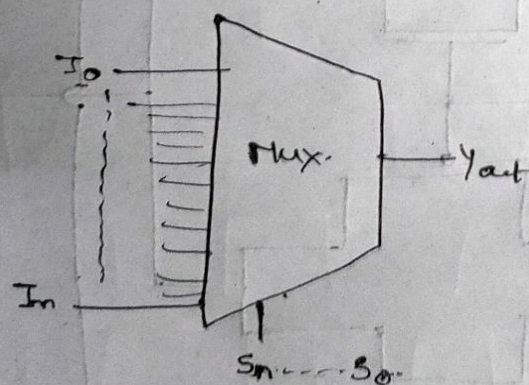


→ AIM : Designing of 4×1 Multiplexer using CMOS Technology in Cadence virtuoso.


→ Introduction :

A Multiplexer is a Combinational circuit that has 2^n input lines and single output line. Simply, the Multiplexer is a Multi-input and Single-output Combinational circuit. The binary information is received from the input lines. On the basis of the values of the selection lines, one of these data inputs will be connected to the output.

Unlike encoder & decoder, there are n selection lines and 2^n input lines. So, there is a total of 2^n possible combinations of inputs. A multiplexer is also treated as Mux.



→ 2x1 Multiplexer

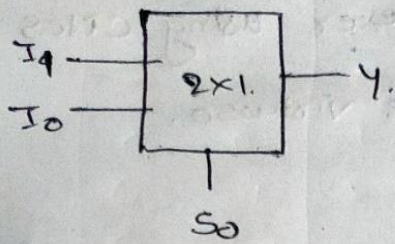


Logic Table


S_0	Y
0	I_0
1	I_1

$$\text{Expression} = \boxed{Y = S_0 \bar{I}_0 + S_0 I_1}$$

2x1 using basic Gates ÷

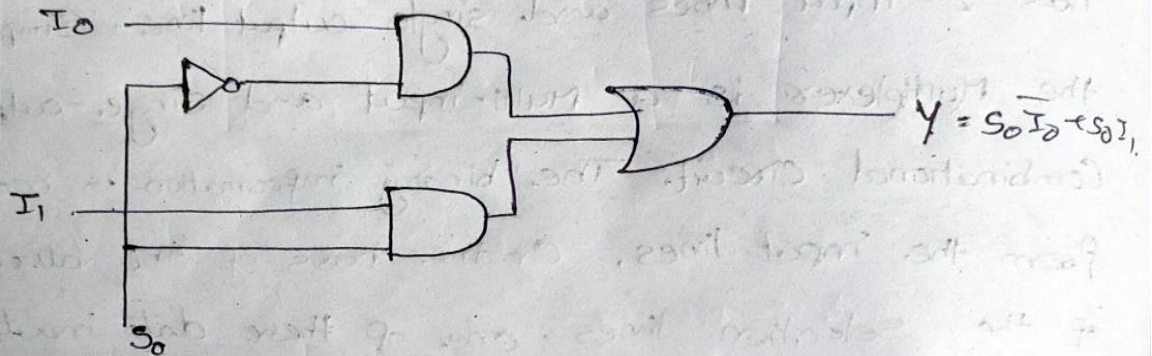


2x1 using CMOS ÷

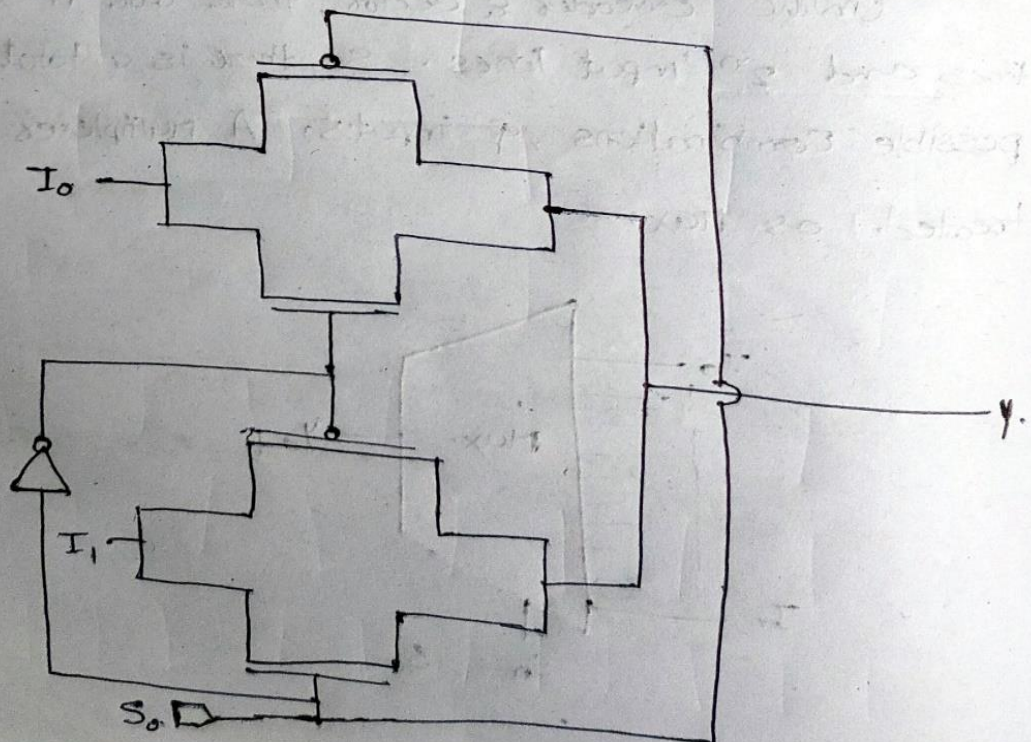

→ Implementation of 4x1 Mux

4x1 Mux

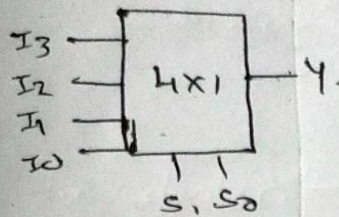


Logic Table


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$$Y = S_1' S_0' I_0 + S_1' S_0 I_1 + S_1 S_0' I_2 + S_1 S_0 I_3$$

4x1 using Basic Gates

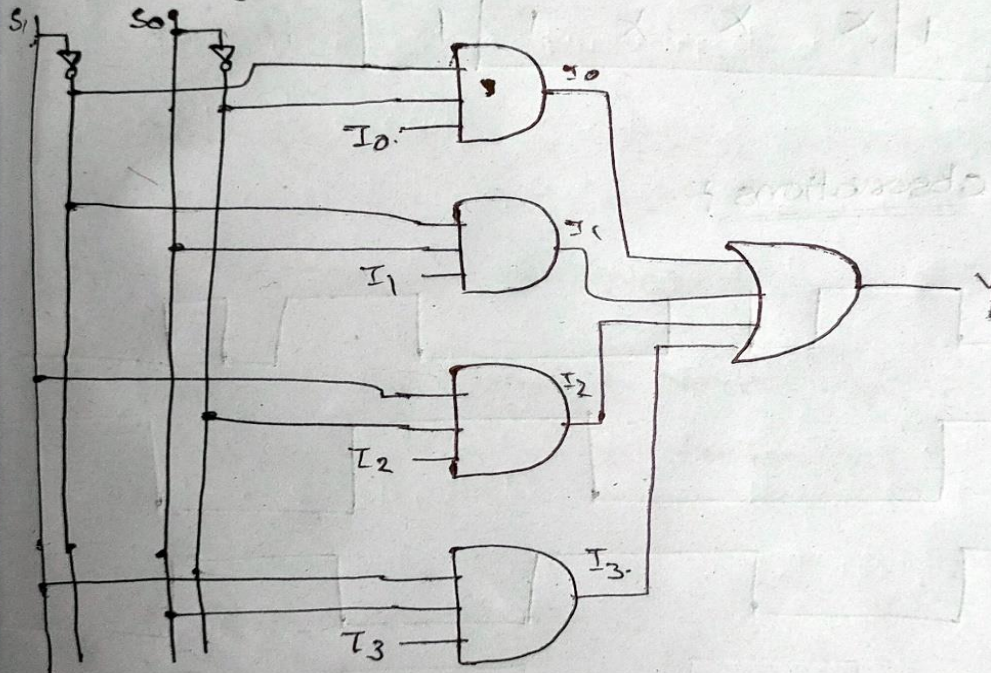


4x1 using 2x1 Mux

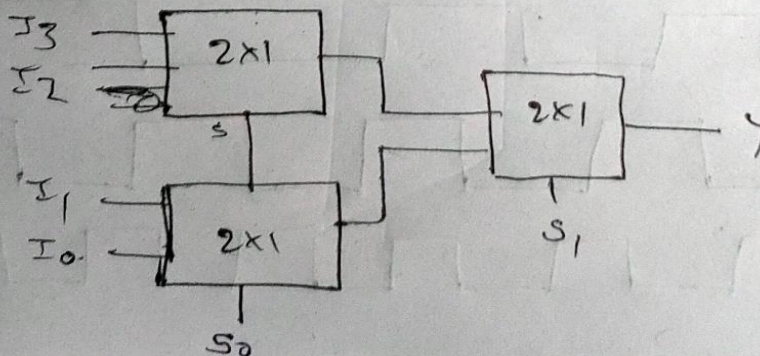

→ characteristic Equation Table.

S_1	S_0	I_0	I_1	I_2	I_3	Y
0	0	0	X	X	X	0
0	0	1	X	X	X	1
0	1	X	0	X	X	0
0	1	X	1	X	X	1
1	0	X	X	0	X	0
1	0	X	X	1	X	1
1	1	X	X	X	0	0
1	1	X	X	X	1	1

Results / observations :

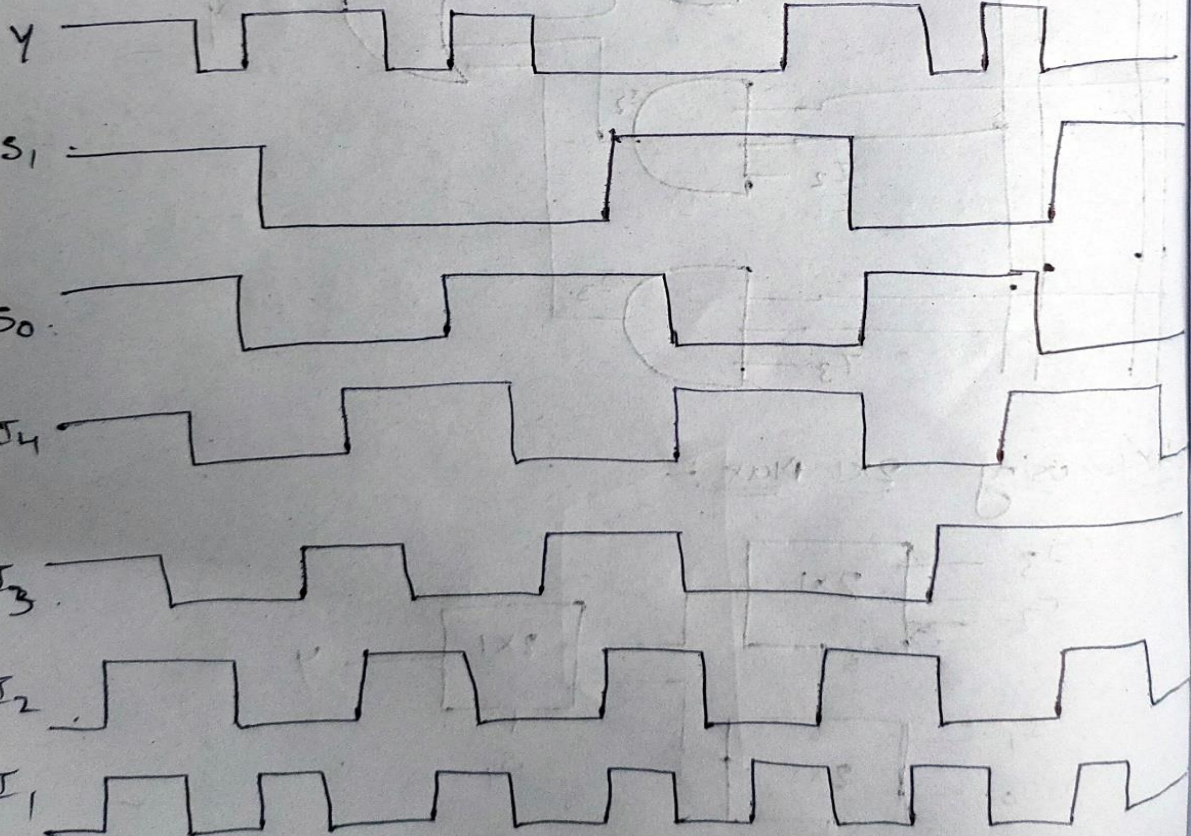

→ Learning Outcomes :

- * We have learned about the Implementation of Multiplexers Using CMOS Technology.
- * working & Functionalities of Multiplexes.
- * Designing of multiplexers in various types like Using Basic gates, using CMOS, & from one mux to another multiplexer.
- * Logic tables & Expressions of Multiplexers.
- * Wave forms of the various multiplexers.



→ Applications of Multiplexers :

- * Multiplexers are used in various applications where multiple data need to be transmitted by using a single line.
- * Communication Systems.
- * Computer Memory & Telephone Networks.
- * Transmission from the Computer System of a Satellite.



Schematics from cadence virtuoso

2*1 mux

12009993-sandeep

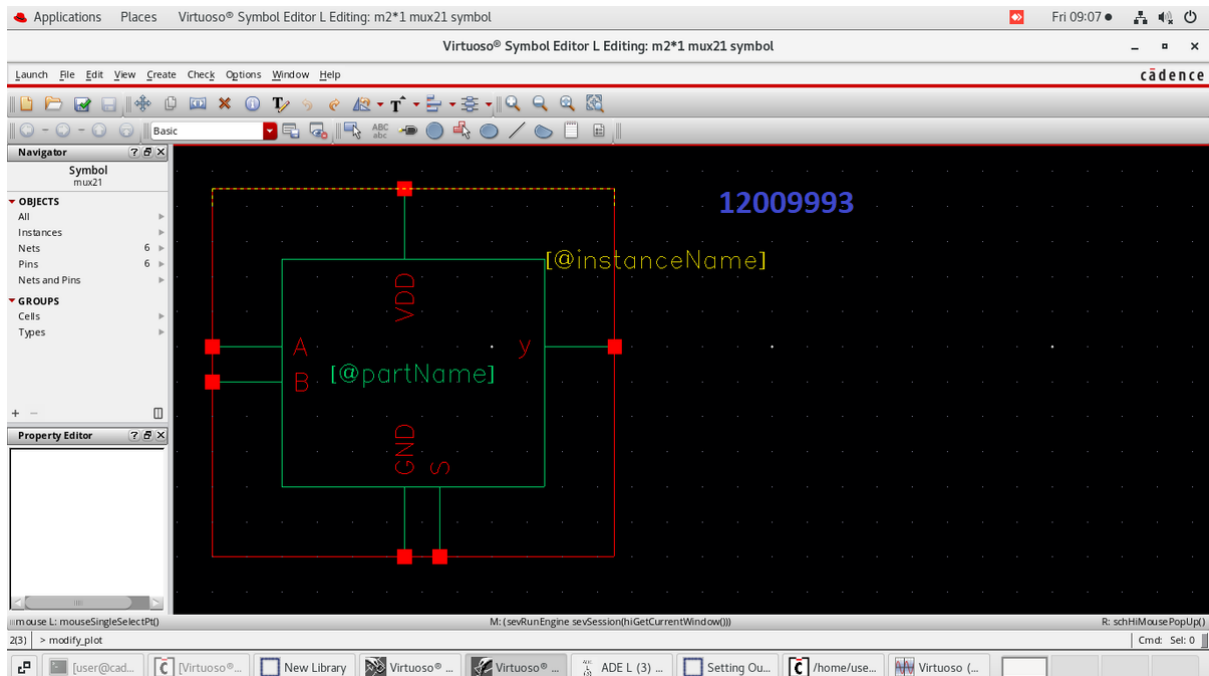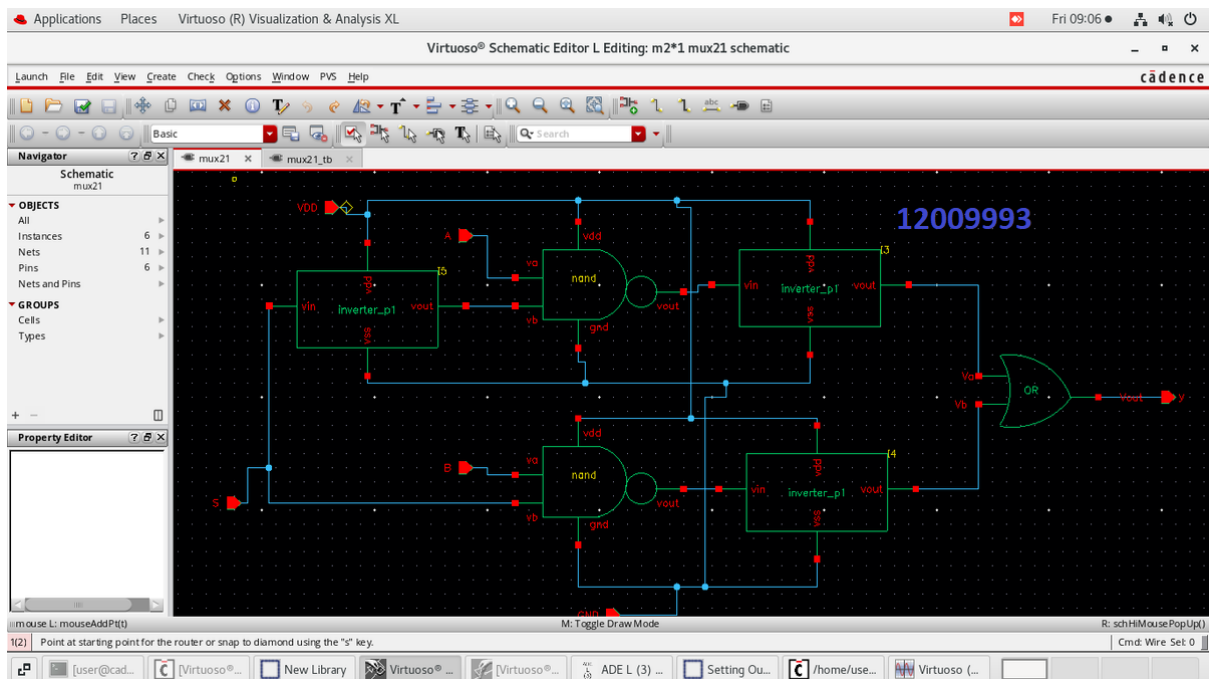

12009993-sandeep

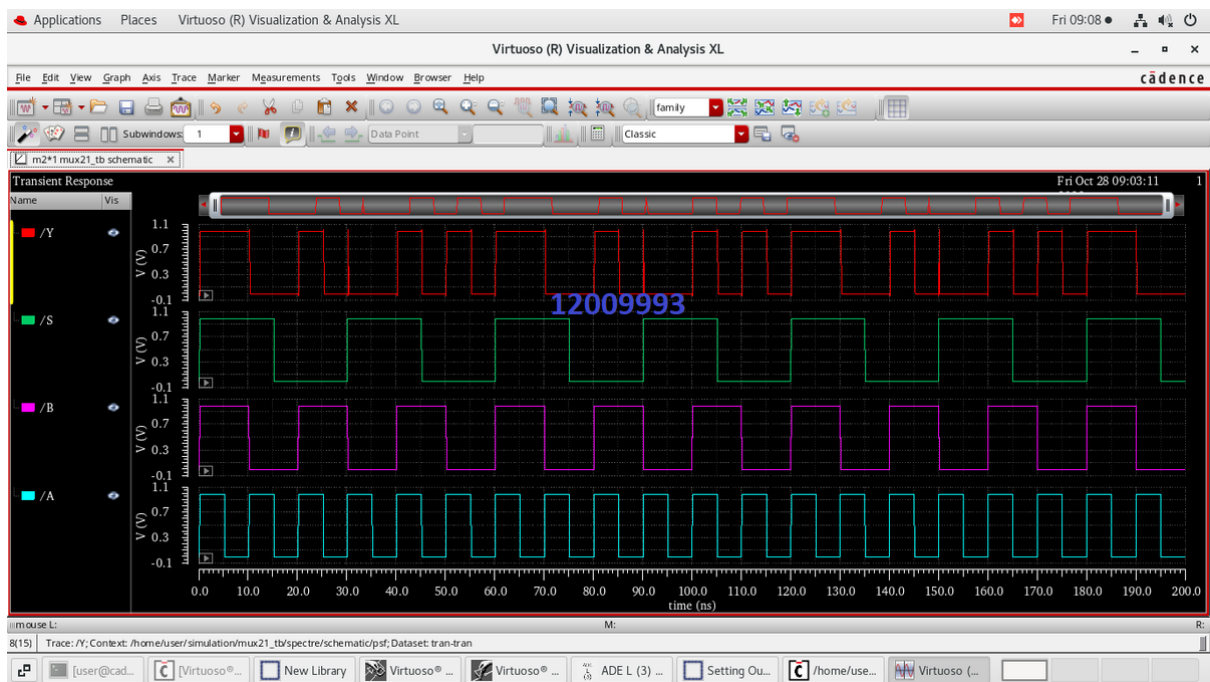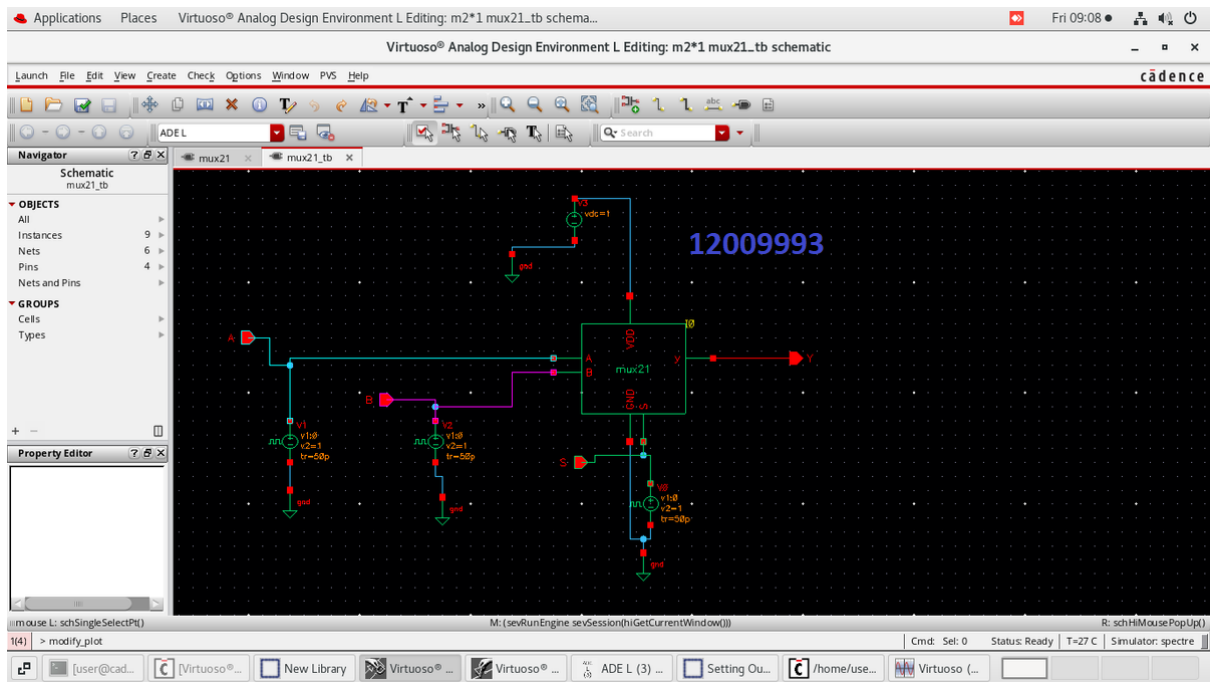

4*1 mux

