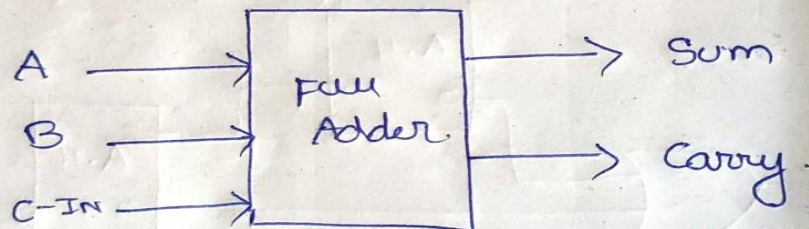


Aim : Designing of 4-bit Fulladder Using CML Technology in Cadence virtuoso.

Introduction :-

Full adder is the adder that adds three inputs and produces two outputs. The first two inputs are A and B and the third input Carry as C_{in} .

A 1-bit full adder adds three operands and generates 2-bit results.



Block Representation.


→ Logic Table :-

A	B	C_{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


→ Gate Representation :

$$\text{Sum} = A \oplus B \oplus \text{Cin.}$$

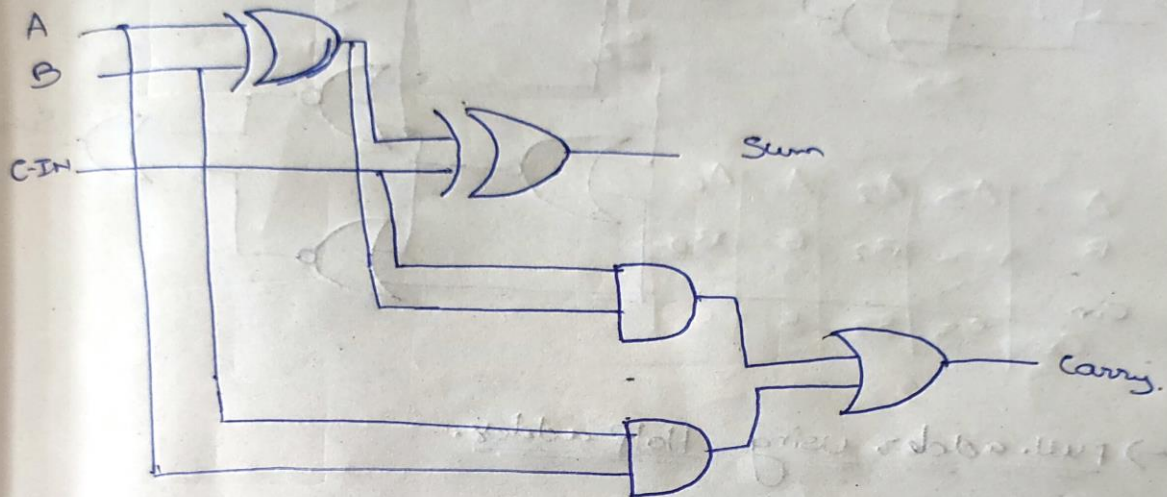
$$\text{Carry} = AB + B\text{Cin} + A\text{Cin.}$$




→ Full adder using NAND Gates :

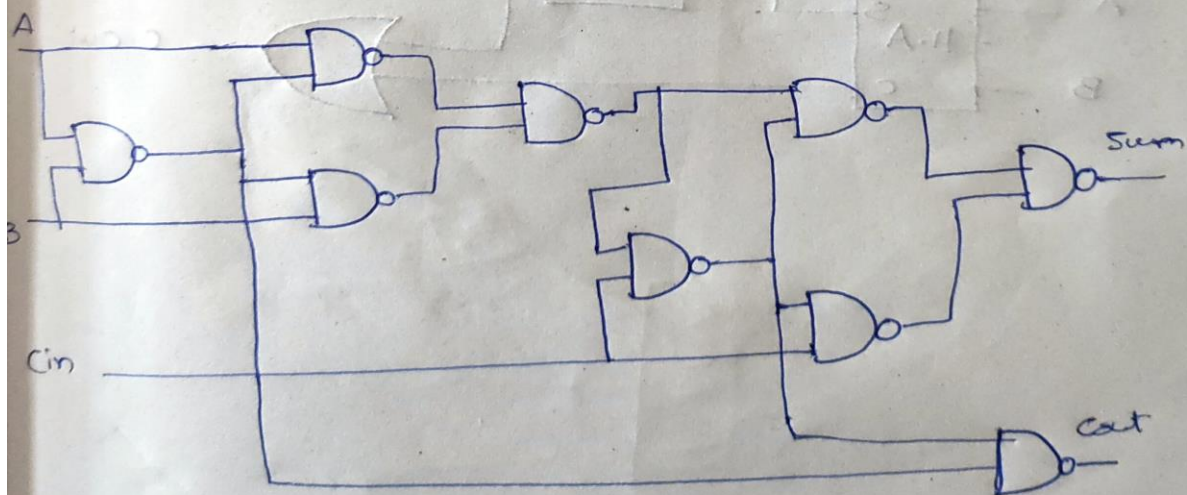


→ Full adder using NOR Gates.

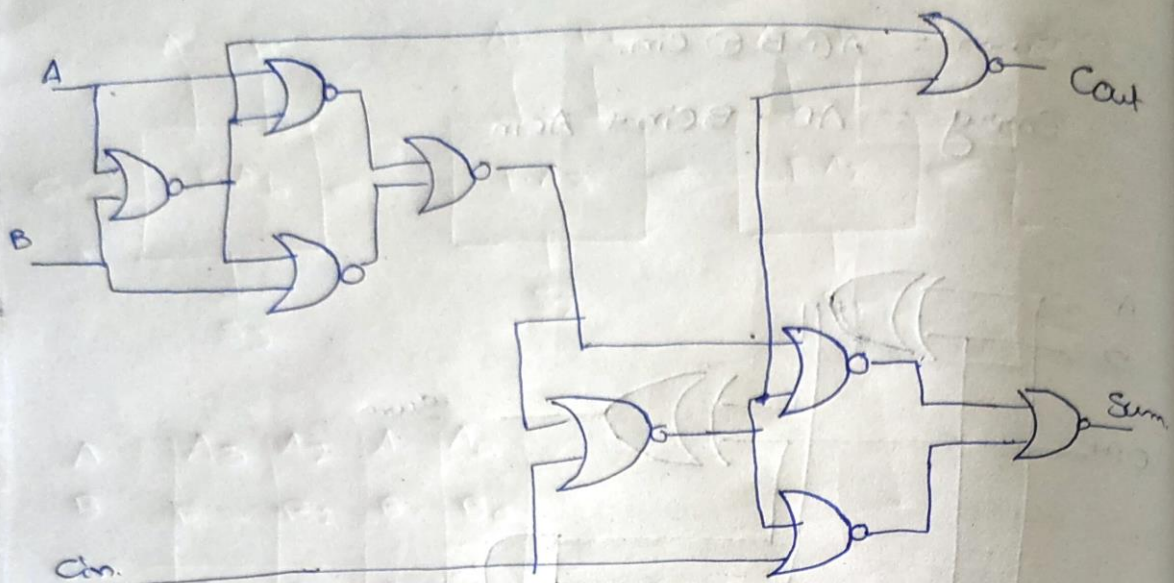


→ Full adder using Half adder.

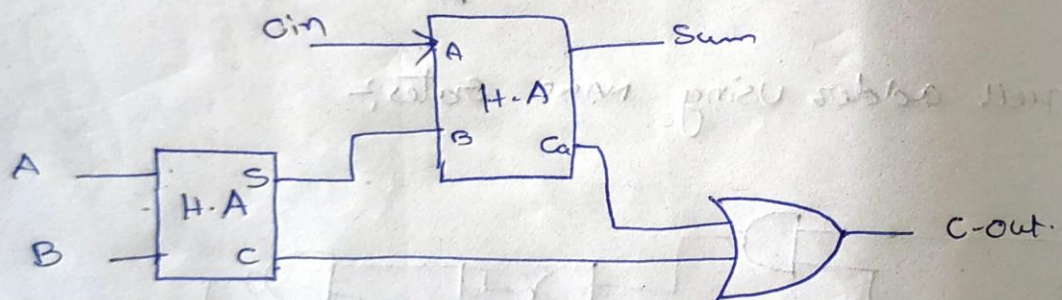

→ Full adder using CMOS Designing.

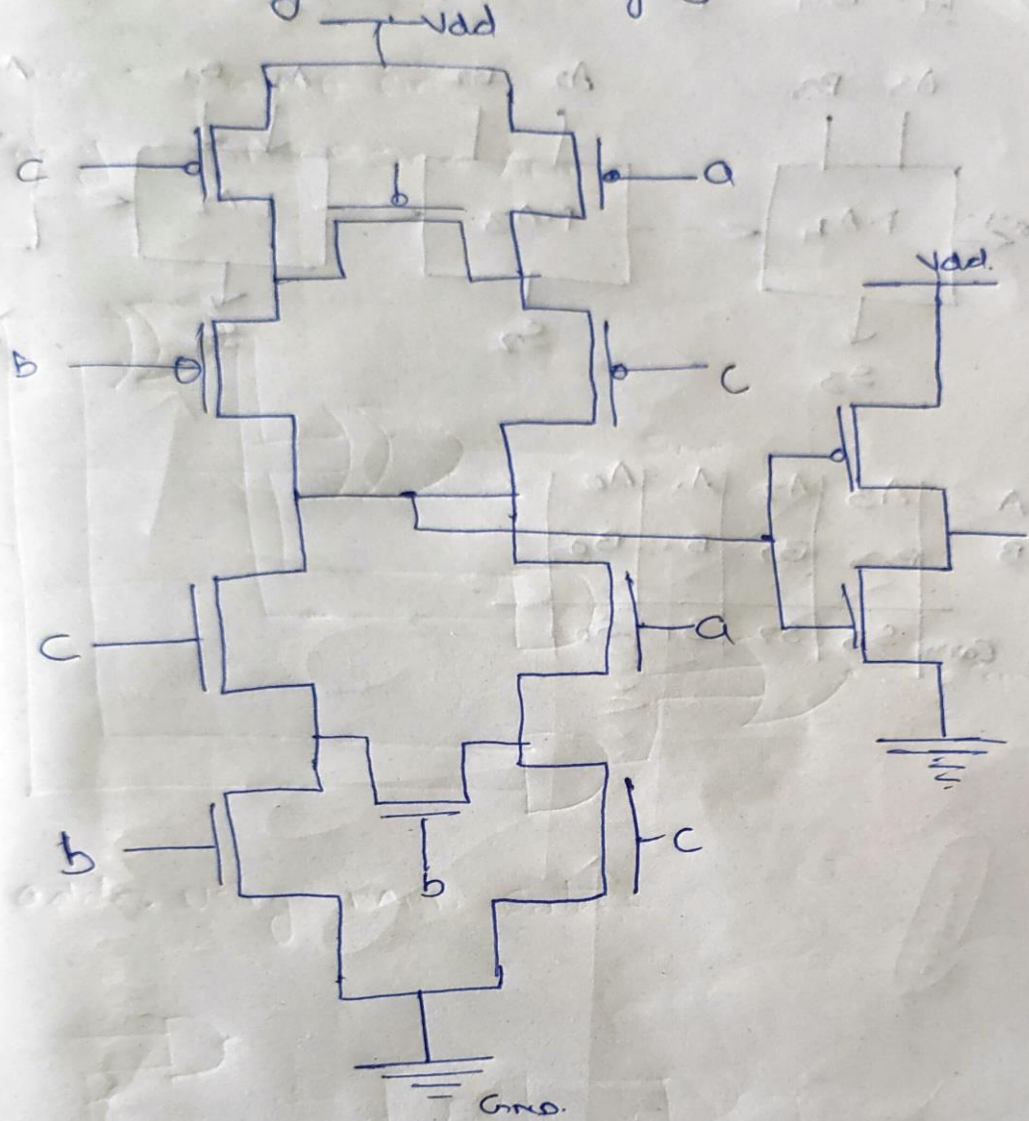


→ 4-bit Full adder Design.

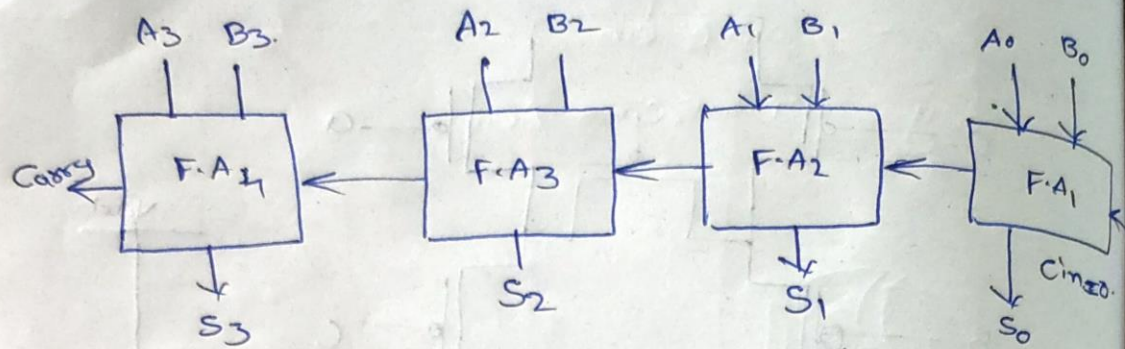

A =	A ₃	A ₂	A ₁	A ₀
B	B ₃	B ₂	B ₁	B ₀
Carry	S ₃	S ₂	S ₁	S ₀

→ 3-Input 4-bit Full Adder.

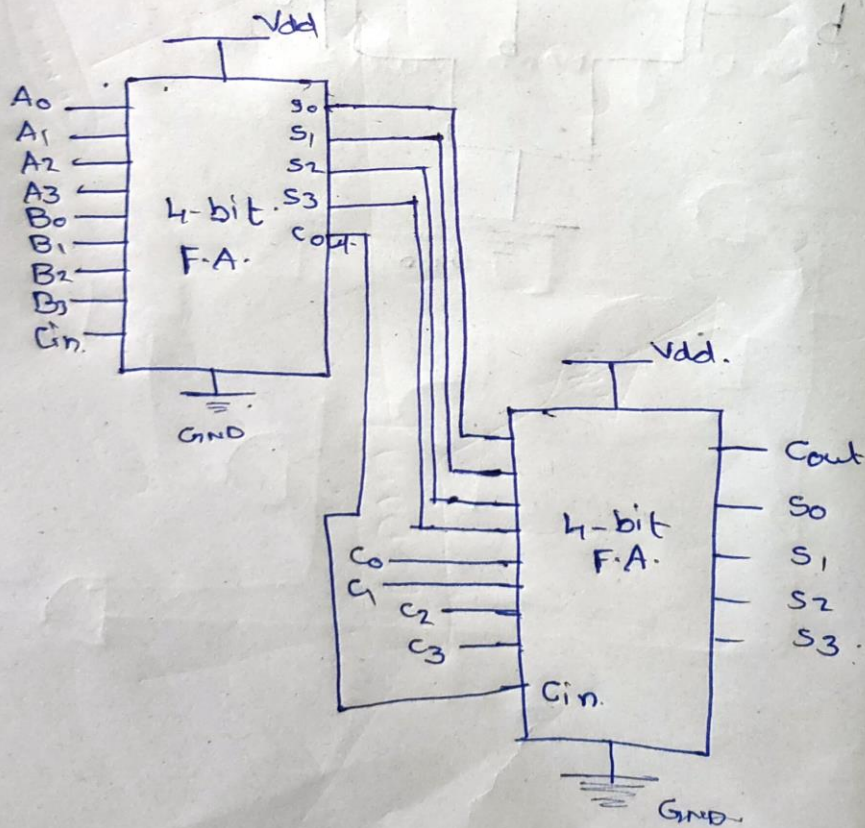


→ Learning Outcomes :-

- * We have understood that how to implement a logic with CMOS.
- * Usage of PMOS & NMOS as pull-up and pull-down networks.
- * Logical Behaviour of Fulladder is known.
- * Designing of n -bit Fulladders using 1bit Full Adders.

→ Applications :-

- * Used in Arithmetic operations.
- * Used in Calculators.
- * Used in various Digital electronics.
- * Used in increment and Decrement operators.
- * It is used to Reduce Complexity of circuits.

12009993

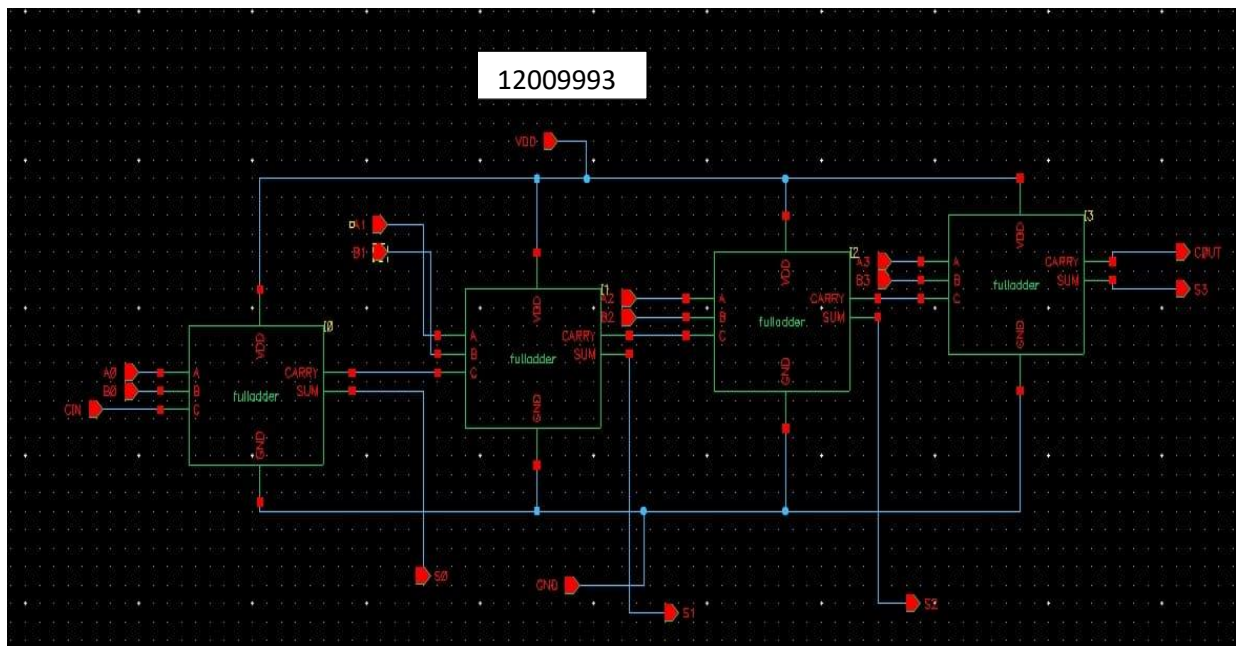

12009993

